

Lab 2: Karnaugh Maps & 2-input NAND/NOR Circuits

Pre-Lab Worksheet #2

NAME: Alexander Williams Lab B 08

1. Karnaugh maps for functions A , M_1 , and M_0

$$C_1 \backslash C_0 R$$

	00	01	11	10
0	0	1	0	0
1	0	0	0	0

A

$$C_1 \backslash C_0 R$$

	00	01	11	10
0	0	1	0	0
1	1	0	1	1

M_1

$$C_1 \backslash C_0 R$$

	00	01	11	10
0	0	1	0	1
1	0	1	0	1

M_0

2. Simplified SOP expressions for M_1 , M_0 and A .

$$A = \bar{C}_1 \bar{C}_2 R$$

$$M_1 = C_1 C_2 + C_1 \bar{R} + \bar{C}_1 \bar{C}_2 R$$

$$M_2 = \bar{C}_2 R + C_2 \bar{R}$$

3. Use Boolean Algebra to ensure that gates with only 2-inputs are needed for M_1 , M_0 and A :


$$A = (\bar{C}_1 \bar{C}_2) R$$

$$M_2 = C_1 (C_2 + \bar{R}) + (\bar{C}_1 \bar{C}_2) R$$

Draw M_1 , M_0 and A using 2-input AND and OR gates and inverters (on the inputs)



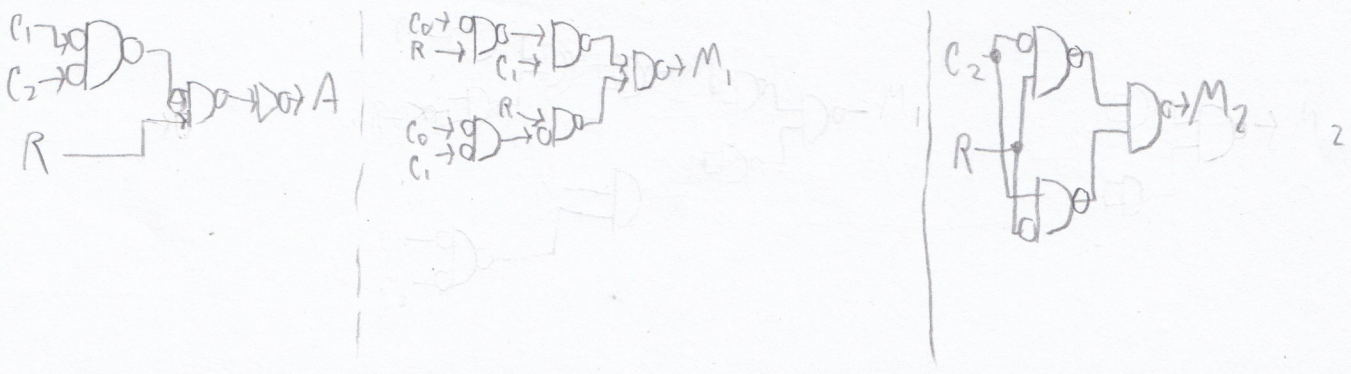Draw M_1 , M_0 and A using 2-input NAND gates and inverters.




4. The SOP of : $F(A,B,C,D) = F(A,B,C,D) = \sum m(5, 8, 12, 13) + \sum d(7, 15)$

$$F(A,B,C,D) = BD + A\bar{C}\bar{D}$$

AB\CD

	00	01	11	10
00				
01		1	X	
11	1	1	X	
10	1			

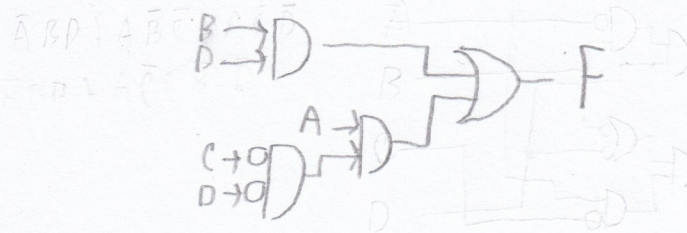5. The circuit that represents the SOP of $F(A,B,C,D)$ using OR gates, AND gates and inverters (on main inputs).




6. The POS of : $F(A,B,C,D) = \sum m(5, 8, 12, 13) + \sum d(7, 15)$

$$F = (\bar{C})(A+B)(A+C+D)(A+B+D)$$


AB\CD

	00	01	11	10
00	0	0	0	0
01	0	1	X	0
11	1	1	X	0
10	1	0	0	0

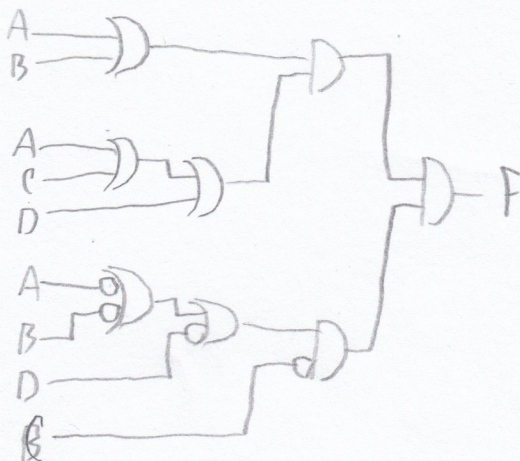7. Draw the POS form of the circuit using 2-input OR and AND gates (plus inverters on the main inputs.)



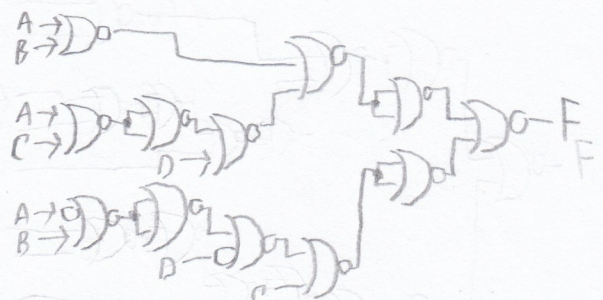8. Re-draw the circuit using only 2-input NOR gates (plus inverters on the main inputs.) Include pin numbers of chips.



Finally, write a list of things that you learned in doing this pre-lab: